

Name:_____ **Student Number:**_____

- 1) a) The PNP transistor of Figure 1 has a $\beta = 100$, $V_{EB} = 0.7 \text{ V}$ and an $I_{CBO} = 10 \text{ nA}$. Find the quiescent I_B , I_C , and V_{CE} .

$I_B =$ _____ $I_C =$ _____ $V_{CE} =$ _____

- b) Sketch the T and π transistor ac models for this circuit.
(Remember to label all components)

T

 π

- c) What is the input impedance, Z_{in} , output impedance, Z_{out} , and the voltage gain, A_v of this transistor amplifier?

$Z_{in} =$ _____ $Z_{out} =$ _____ $A_V =$ _____

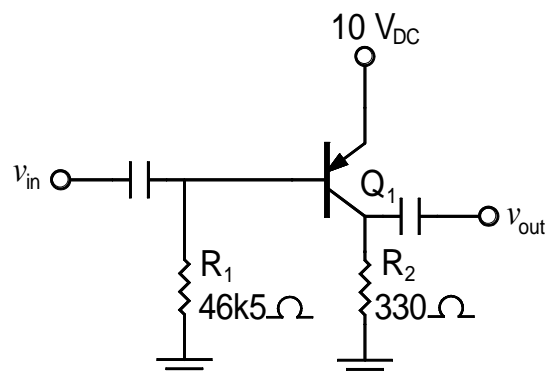


Figure 1

Name:_____ **Student Number:**_____

Name: _____ Student Number: _____

2) The transistor in Figure 2 has a $\beta = 100$, $V_{BE} = 0.7 \text{ V}$, and an $I_{CBO} = 10 \text{ nA}$.
The Schottky diode has a forward voltage drop of 0.4 V .

a) Find the currents I_B , I_C , and I_D .

$I_B =$ _____ $I_C =$ _____ $I_D =$ _____

b) Is the transistor active, saturated or in cutoff?

Active ☐

Saturated ☐

Cutoff ☐

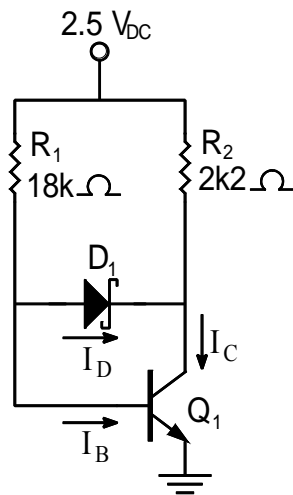


Figure 2

Name:_____ **Student Number:**_____

Name: _____ Student Number: _____

3) The transistors in Figure 3 both have a $\beta = 100$, $V_{BE} = 0.7 \text{ V}$, and an $I_{CBO} = 10 \text{ nA}$.

a) Determine v_{out} and v_e with $v_{in} = 0 \text{ V}$.

$v_{out} =$ _____ $v_e =$ _____

b) What level does v_{in} have to be to just switch Q_1 ON?

In this condition, what state is Q_2 and the resulting v_{out} ?

$v_{in} =$ _____ Q_2 State = _____ $v_{out} =$ _____

c) Starting with the condition of part b, what level does v_{in} need to be to just switch Q_1 OFF?

$v_{in} =$ _____

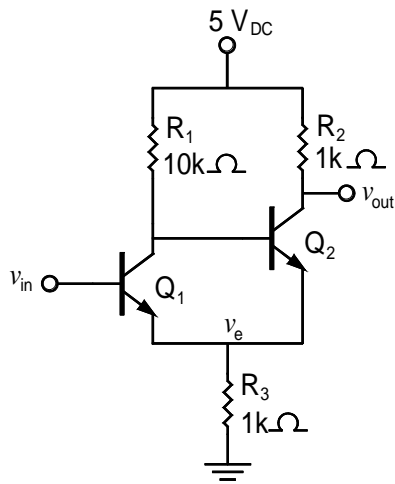


Figure 3

Name:_____ **Student Number:**_____

4) a) For the two stage amplifier shown in Figure 4, calculate the input impedance, Z_{in} , output impedance, Z_{out} , and the overall voltage gain $A_{V(Total)}$.

Assume $\beta = 100$, $|V_{BE}| = 0.7V$, $V_{CE(sat)} = 0.3\text{ V}$, $I_{CBO} = 0$, and that the amplifiers are biased properly.

$Z_{in} =$ _____

$Z_{out} =$ _____

$A_{V(Total)} =$ _____

b) Consider the situation where a generator with a source resistance of $990\ \Omega$ was connected to the input and an external $10\text{ k}\Omega$ load was connected to the output.

What would the output voltage be in volts peak to peak if the generator was set for a level of 10 mV_{RMS} ?

$v_{out} =$ _____

V_{P-P}


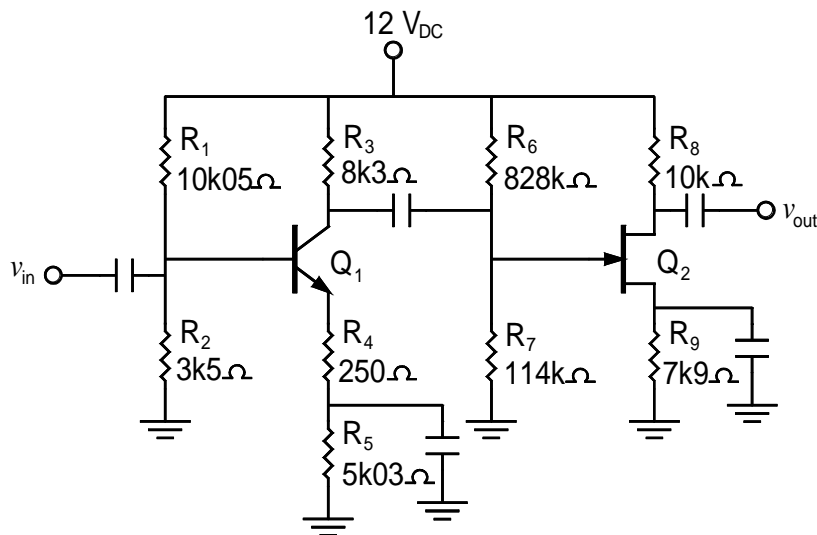


Figure 4

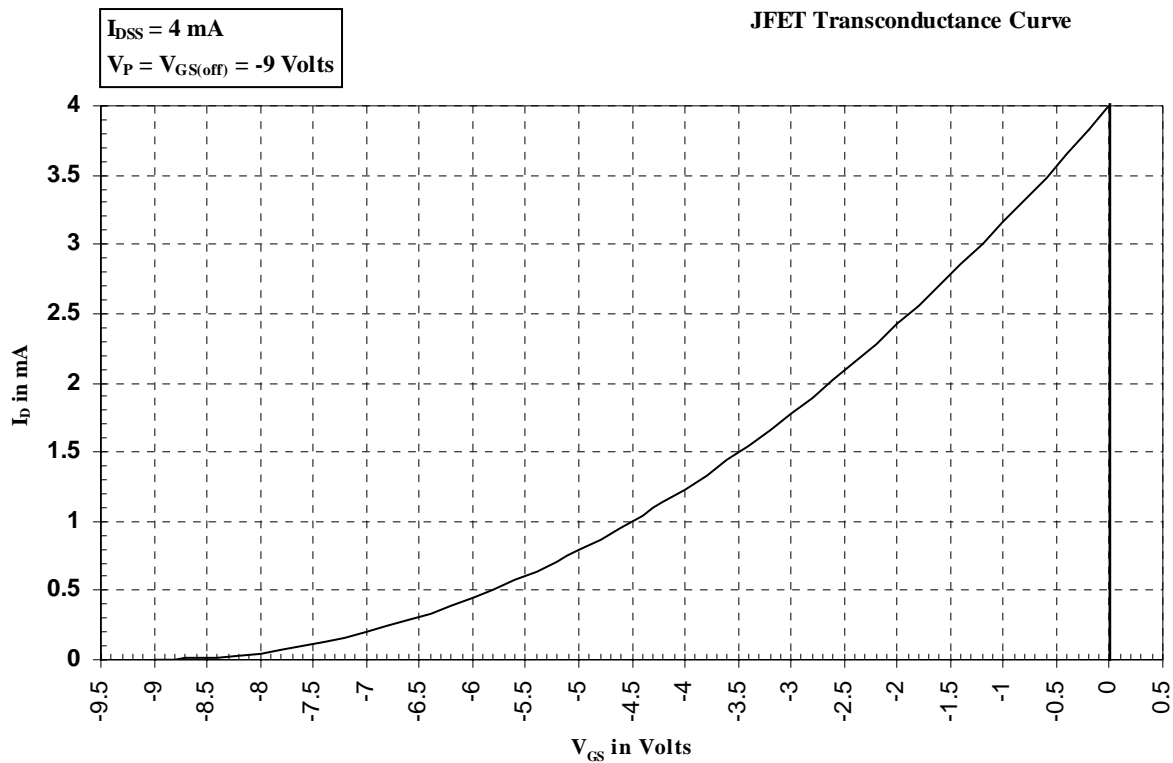

Name:_____ **Student Number:**_____

Name: _____ Student Number: _____

5) For the circuit shown in Figure 5, calculate the voltage v_o and the current i_o with a source voltage, v_s , of 3 V.

Note: Assume an ideal operational amplifier.

$v_o =$ _____

$i_o =$ _____

What direction is the output current, i_o , flowing?

(Note: Your calculations should support your answer. i.e. No guessing is allowed)

Into Op-amp ☐ Out of Op-amp ☐

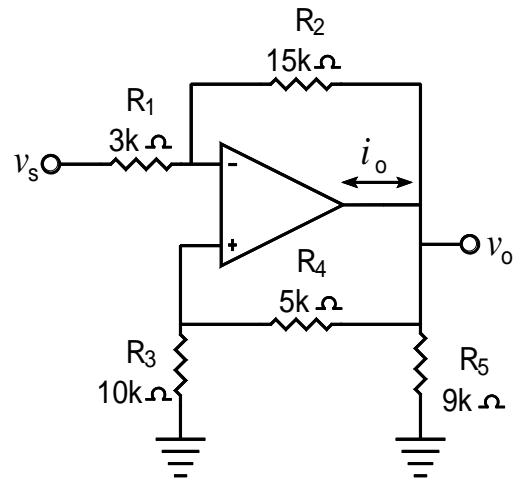


Figure 5

Name:_____ **Student Number:**_____